

Please check that this question paper contains 09 questions and 02 printed pages within first ten

[Total No. of Questions: 09]

[Total No. of Pages: 02]

Uni. Roll No. ....

Program: B.Tech.(Batch 2018 onward)

Semester: 4<sup>th</sup>

Name of Subject: Digital Electronics

Subject Code: PCEE-105

Paper ID: 16186

Scientific calculator is Allowed

MORNING  
19 SEP 2022

**Time Allowed: 03 Hours**

**Max. Marks: 60**

**NOTE:**

- 1) Parts A and B are compulsory
- 2) Part-C has Two Questions Q8 and Q9. Both are compulsory, but with internal choice
- 3) Any missing data may be assumed appropriately

**Part – A**

**[Marks: 02 each]**

**Q1.**

- a) Prove that  $AB + ABC + A\bar{B} = A$
- b) What are shift registers? Give applications
- c) Which is the fastest analog digital converter and why?
- d) Comparison EPROM and EEPROM.
- e) Define demultiplexer.
- f) Convert hexadecimal number  $(4C8.2)_{16}$  into its equivalent decimal number.

**Part – B**

**[Marks: 04 each]**

- Q2.** Realize OR, AND, NOT, NOR gates using NAND gate only.
- Q3.** Using K map realize the following expression using minimum number of gates.  
$$Y = \sum m(1, 3, 4, 5, 7, 9, 11, 13, 15)$$
- Q4.** Write a short note on ring counter.
- Q5.** Give classification of memories based on principle of operation.
- Q6.** Describe the working of R2R ladder type D/A converter.
- Q7.** Explain step by step the design of full adder using two half adder and one OR gate.

**Part – C**

**[Marks: 12 each]**

- Q8.** 1. Make a K map for the function  $f = AB + A\bar{C} + C + AD + A\bar{B}C + ABC$   
2. Express  $f$  in Canonical SOP form  
3. Minimize it and realize the minimized expression using NAND gates only.

or

Describe edge triggered JK Flip Flop with the help neat waveforms and truth table.

- Q9.** Explain the architecture and function of programmable arrays.

or

Draw the circuit of a dual slope A/D converter and explain its operation. Also write advantages and disadvantages.

\*\*\*\*\*

MORNING  
19 SEP 2022